

---

## EE371 Debug Examples

Intel Corporation  
jstinson@mipos2.intel.com

## Agenda

---

- Speedpath Failure
- Circuit Marginality: Noise
- Functional Failure
- Circuit Marginality: Multiple
- PowerUp Problems

## Speedpath Failure

## Speedpath Example: The Wall Shmoo

Voltage

d004508A16588 -- #FF005 (92C)

```
3.2V | EEEEEEEE ++++++
3.0V | EEEEEEEE ++++++
2.8V | XEEEEEEE ++++++
2.6V | XXEEEEEE ++++++
2.4V | XXXXXEEE ++++++
2.2V | XXXXXXXE ++++++
2.0V | XXXXXXXXX ++++++
```

Passing Region

```
+ ^ - - - - ^ - - - - ^ - - - - ^ - - - -
  10.0  11.2  12.4  13.6
+ - pass
E - Wall fail
X - other fail
```

Bus Period

## Skew Insensitive wall

d004508A16588 -- #FF005 (92C)

```
3.2V | EEEEEEEE+++++
3.0V | EEEEEEEE+++++
2.8V | XEEEEEEE+++++
2.6V | XXEEEEEE+++++
2.4V | XXXXXXEEE+++++
2.2V | XXXXXXXXE+++++
2.0V | XXXXXXXXXX+++++
      +^-----^-----^-----^--
          10.0  11.2  12.4  13.6
+ - pass
E - Wall fail
X - other fail
```

### Fast Transistor Part

d004508A16588 -- #SS131 (92C)

```
3.2V | XXXXXEEE+++++
3.0V | XXXXXXEE+++++
2.8V | XXXXXXXXE+++++
2.6V | XXXXXXXXXX+++++
2.4V | XXXXXXXXXX+++++
2.2V | XXXXXXXXXXXXXXX+++++
2.0V | XXXXXXXXXXXXXXX+++++
      +^-----^-----^-----^--
          10.0  11.2  12.4  13.6
+ - pass
E - Wall fail
X - other fail
```

### Slow Transistor Part


## The Wall Debug

- Production test platform suspected
  - A timing setup problem
  - How could silicon act this way?

## However...

- Debug test platform confirmed
  - Unlikely two diff't platforms had same timing error
  - Now we had to do the debug...

## Pattern Timeline

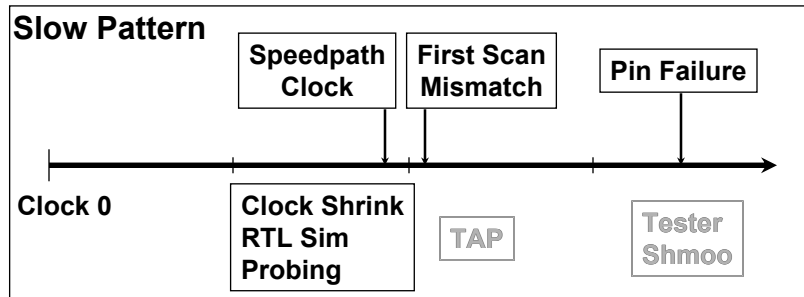


## Debug Process


## Why was it a wall?

- Long Interconnect Line
  - RC Delay less sensitive to driver strength
  - Voltage/process only improve driver

## Interconnect Effect

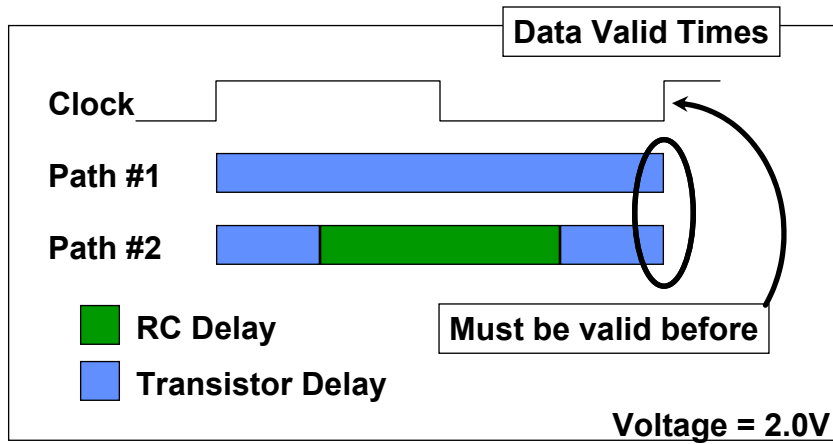


## Interconnect Effect

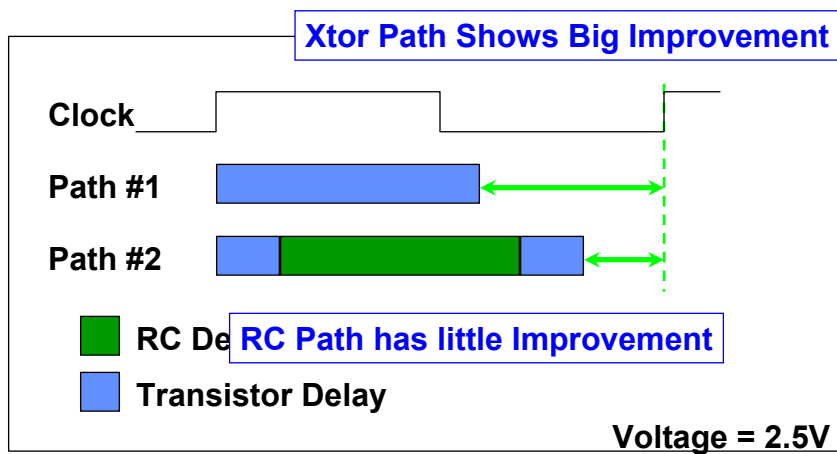
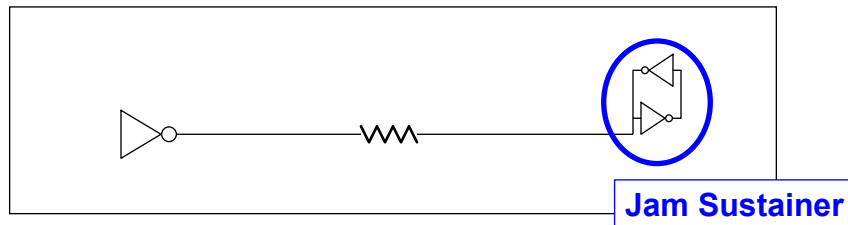
## Why was it a wall?

- Jam sustainer at end of the line
  - Fights transition of signal
  - Sustainer gets stronger with voltage/skew
  - Adds to “wall” characteristics



## Wall Follow-up

- Two FIB experiments
  - Driver speedup – wall moved
  - Cut sustainer – wall “leaned”

## Shmoo with Cut Sustainer

```
d004508A16588 -- #FF013 FIB
3.2V | EEEE+++++
3.0V | EEEEE+++
2.8V | XEEEE+++++
2.6V | XXEEEE+
2.4V | XXXXXEE+
2.2V | XXXXXXXXE+
2.0V | XXXXXXXXXX+
      +^-----^-----^-----^---
        10.0  11.2  12.4  13.6
+ - pass
E - Wall fail
X - other fail
```

Wall has leaned over

## Circuit Marginality: Noise

## Noise Example

```
g196027*, part#ZC-106
3.3V | BCCCCCCCCC
3.2V | BCBBCCCCCC
3.1V | BBBBBBBBBBB
3.0V | BBBBBBBBBBB
2.9V | BBBBBBBBBBB
2.8V | BBBBBBBBBBB
2.7V | BBBBBBBBBBB
2.6V | BBBBBBBBBBB
2.5V | BBBBBBBBBBB
2.4V | +B+BBBBBBB
2.3V | ++++BB+++BB
2.2V | ++++++
2.1V | ++++++
2.0V | A+++++
      +^-----^-----
      10.0 16.0
      + - pass
```

- High Voltage Failure
  - Only one FAB showed signature
    - Second FAB seemed clean
  - Scan pointed to branch memory array



Pass Low Voltage Only

## Noise Debug



- EBeam confirmed branch array read
  - Visibility limited in array
- Bit 4 resolved later than other bits
  - Based on EBeam waveforms
- Signals on either side of read lines transistioned in opposite direction
  - Suspected coupling problem



## Coupling Schematics

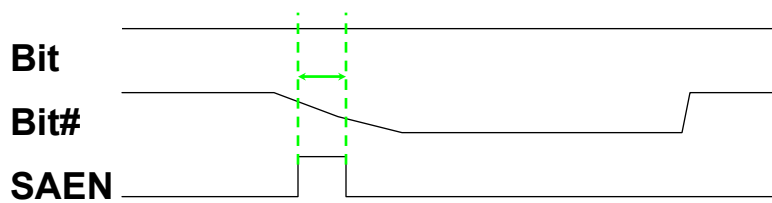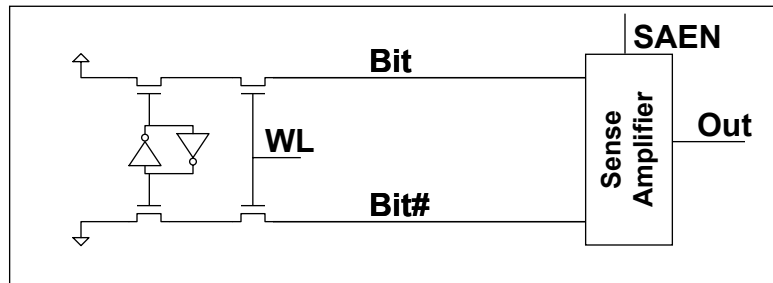

## Coupling Schematics

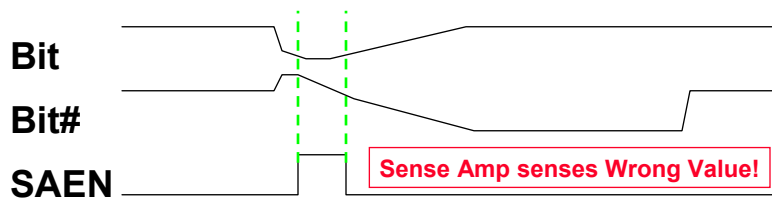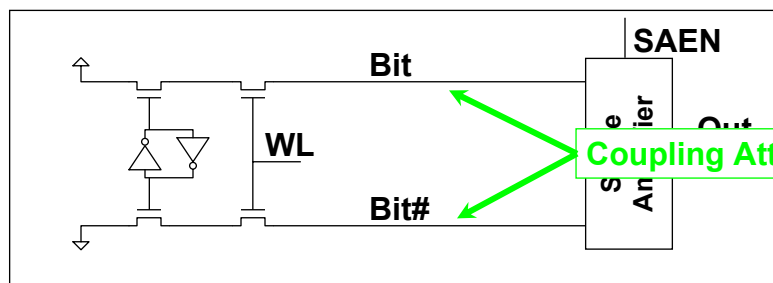

## BTB Coupling Debug

---



- Parameters data checked at problematic FAB
  - M2 CD's wider than normal
  - ILD1 and ILD2 thicker than normal
  - More sensitive to coupling
- Audit of original design
  - Simulations ignored some coupling
  - New simulations showed failure

## BTB Coupling Validation: FIB experiments

---

- Deposit extra capacitance on read line
  - Resists coupling from neighbors
- Extend sense amp pulse width
  - Gives more time for read to resolve

## Coupling Schematics

 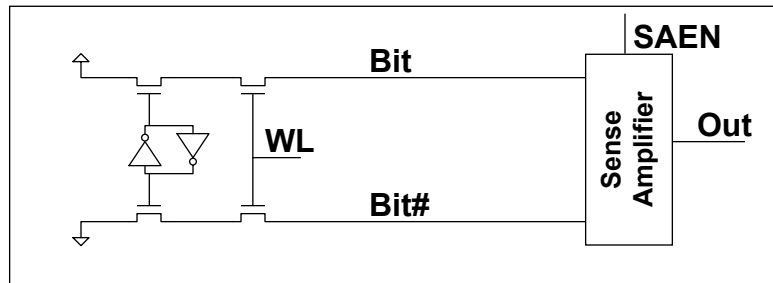

## Functionality Failure

## Functionality Problem

---

- “Dash stepping” first silicon non-functional
  - Stepping was supposed to fix a min-delay race
- Suspected inadequate race fix
  - Scandiff confirmed same circuitry
  - EBeam also confirmed...
  - But visibility was limited

## Functionality Debug


---

- Design team was confident in fix, so...
- Plan to strip back the entire block
  - Look for possible mask defect
  - Takes 4-10 days in FIB


### However...

- Noticed a floating node in EBeam scope

## Floating Node

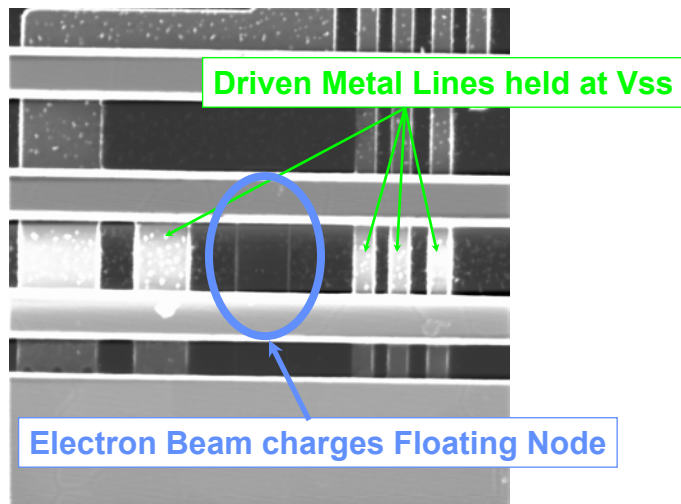

## Floating Node

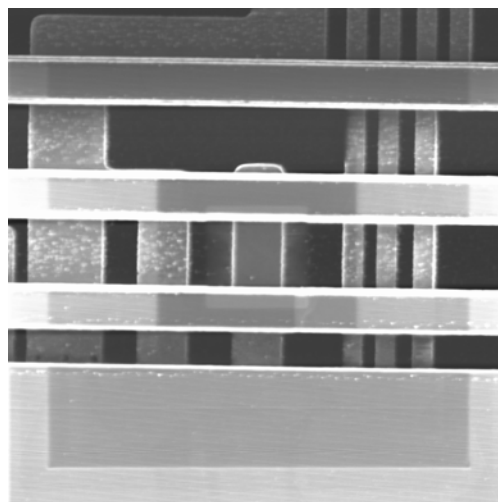


## Floating Node Debug

---

- Node should NOT have been floating
- A0 and A1 layout compared
  - Via1 or M1 could cause error
- FIB strip back focused on this node

## FIB Stripback Results


---

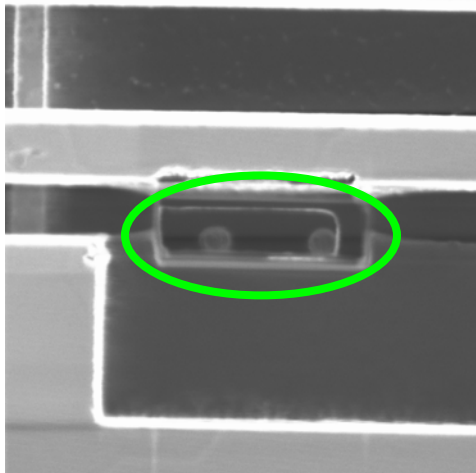

- **Should be 3 via1's**
- **FAB contacted**
  - Accidentally used A0 via1 mask
- **Problem fixed**
  - New silicon arrived shortly

## FIB Stripback Results

---

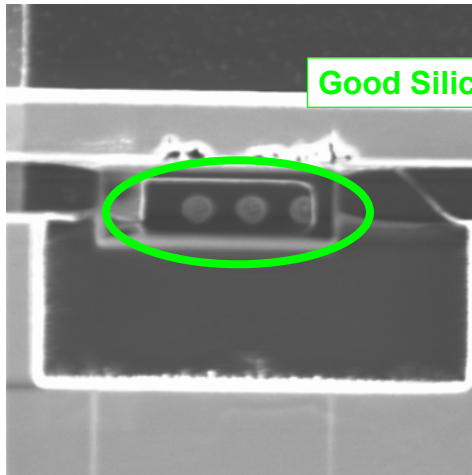

Good Silicon has all 3 via1's

- Fully functional with correct via1 mask

## Functionality Summary

---

- Notice details
  - Focused stripback saved days of work
  - Very important during time critical debug

## Circuit Marginality: Multiple Sources

---


## Circuit Marginality

---

- Observed High Vcc failures
  - Frequency Insensitive
- TDO only failure
  - All signature mode tests were failing
  - Turning off signature mode allowed test to pass





## High Vcc Shmoo

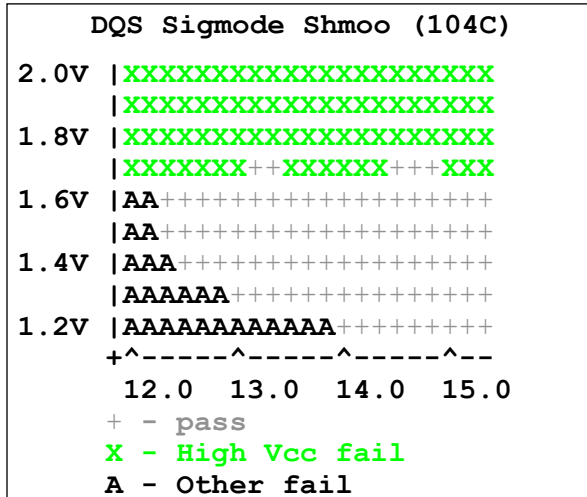



## Marginality Root Cause

- Scanout stopped working in failure region
  - Deduce scan chain itself was broken
- Probing was only way to root cause
  - Laser Voltage Probe was able to narrow failure down to Scan MSFF
  - Three different mechanisms observed


## Scan MSFF Analysis: Pass

 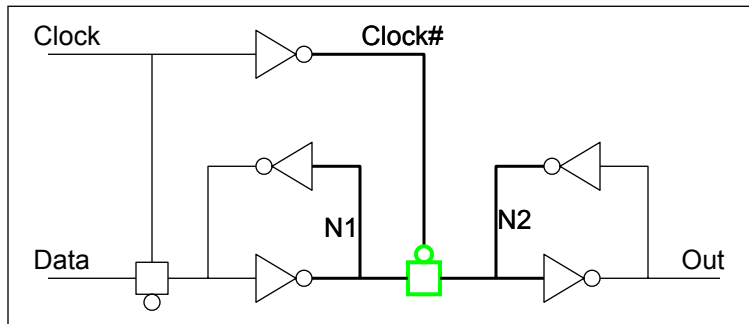


## Problem #1: Charge-Share

 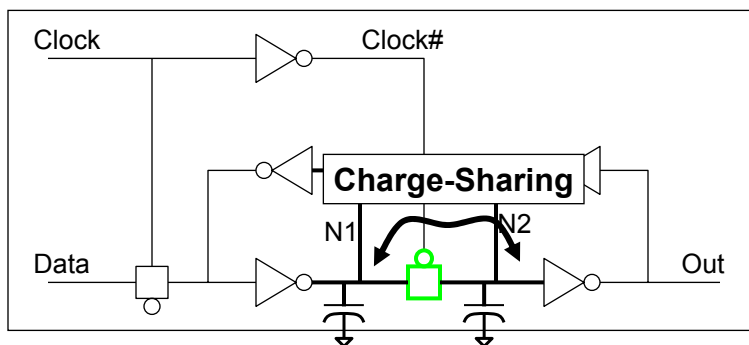

## MSFF Problem #2

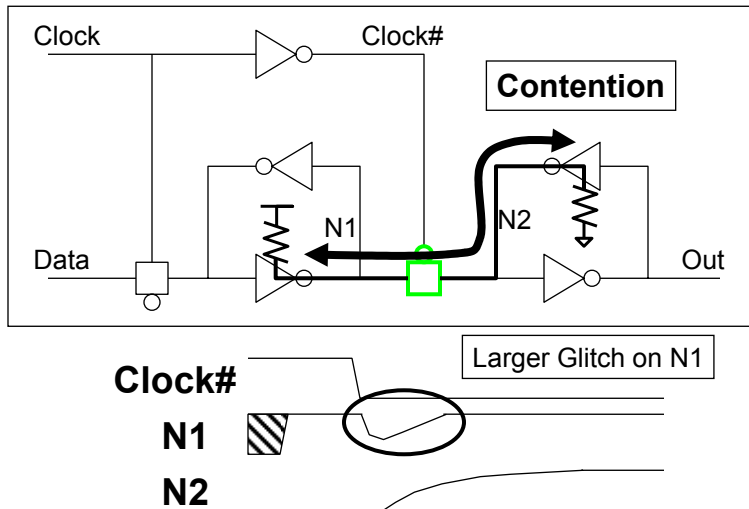

## MSFF Problem #3

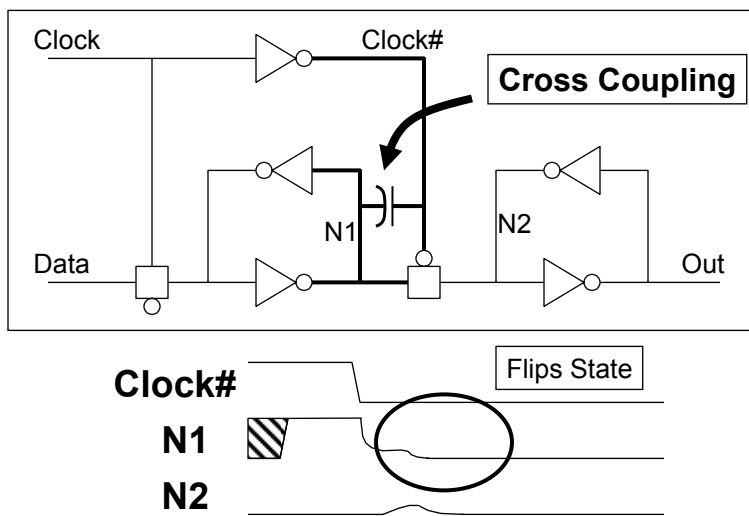

## Scan MSFF “Backwriting”

---

- Slave “backwrites” value into Master
  - Combination of three mechanisms to cause failure
- Re-simulated all standard cell MSFF’s
  - Two other cells flagged with same problem
- Circuit was a direct “shrink” from a previous process
  - Discovered same issue on prior process—but at a MUCH higher voltage


## PowerUp and Initialization

---


## PowerUp Issue

- Observed *\*some\** systems wouldn't boot
  - Toggling RESET always enabled boot
  - Toggling power did not guarantee boot
- Nasty problem to debug
  - System level issue (not seen on tester)
  - Intermittent failure (occurred 1 out of 100 times)
  - Debug tools not enabled (part hasn't booted)
- Started with oscilloscope waveforms...

## Oscope Waveforms

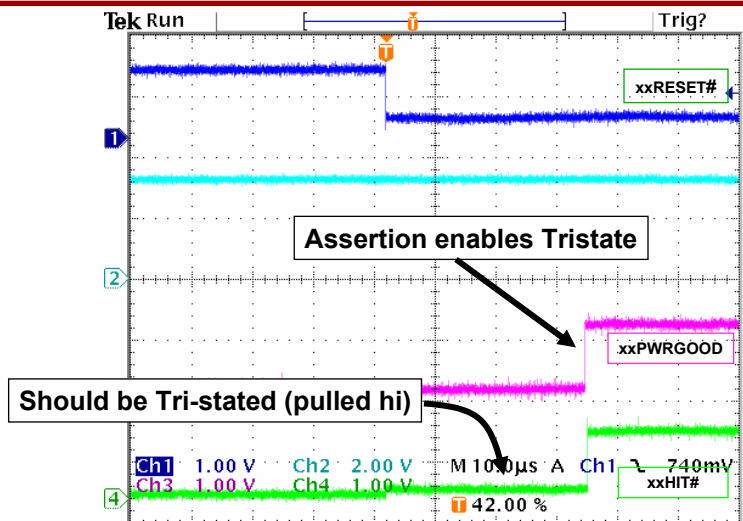
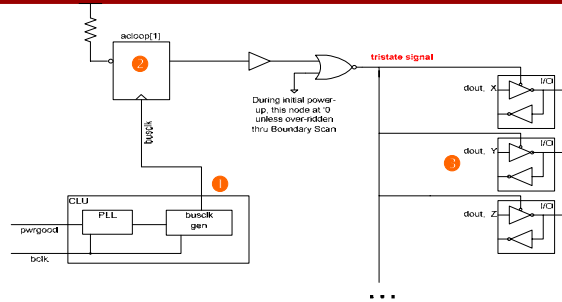
## Why is TriState determined by PWRGOOD?




- Discovered busclk dependency @ 2
  - ACLOOP[1] directly controls I/O tristate signal
    - Depends upon busclk for proper initialization
  - While !PWRGOOD, busclk is not generated
    - Power-up initialization @ 1 may generate a busclk → no issue
    - Otherwise, must depend on power-up initialization of ACLOOP[1] (2)
    - “Driven value” on I/O pins will depend on power-up initialization at 3

## Why wasn't the part booting?

- PWRGOOD will always clear the ACLOOP
  - Eventually the pins should tristate
  - So, why was the part still not booting?
- Further characterization: Power levels were very low
  - When the part failed to boot, the power was very low
  - Potentially indicated that the PLL wasn't running
  - Discovered secondary effect of ACLOOP initialization problem

## PLL Ratio Depends on PWRGOOD

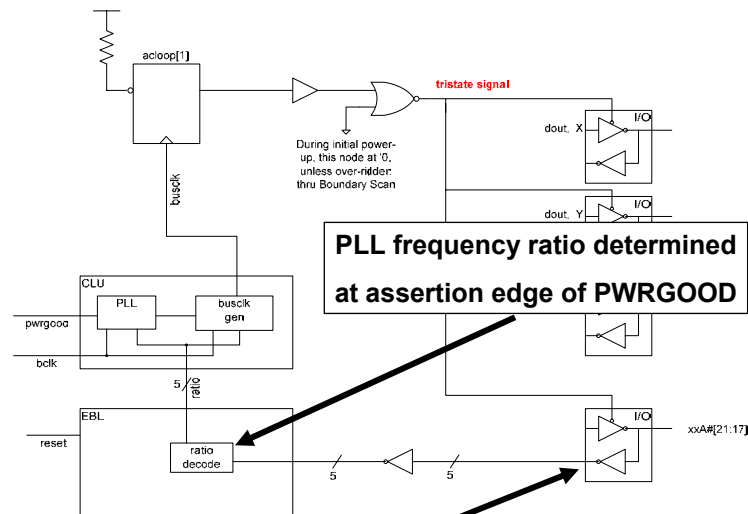

J. Stinson © 2007

45

## Final Root Cause

- System drives address pins at PWRGOOD assertion
  - Sets internal PLL frequency
  - Address pins are \*supposed\* to be tristated by the processor
- If ACLOOP powers up incorrectly, contention can occur
  - Processor is driving a '0' on address pin; system is driving a '1'
  - The processor will always win
- PWRGOOD assertion tristates the address bus
  - Too late! It's already been sampled by PWRGOOD assertion
  - Only "illegal" bus fractions will cause failure
    - Only 7 out of 32 possible bus fractions are "illegal"
- Failure requires a confluence of diff't events
  - ACLOOP powers up "on"
  - Bus clock does NOT glitch during power up
  - Address pins power up driving an "illegal" bus fraction

J. Stinson © 2007


EE 371: Debug Examples

46

## 2<sup>nd</sup> PowerUp Issue


- Observed *\*some\** systems wouldn't boot
  - Toggling RESET never enabled boot
  - Toggling power usually enabled boot
- Nasty problem to debug
  - Intermittent failure (occurred 1 out of 1000+ times)
- Some bright spots
  - Able to demonstrate on tester
    - Enabled "deterministic" behavior
    - Enabled debug tools (scan)

## Vcc Shmoo (100x repeat)

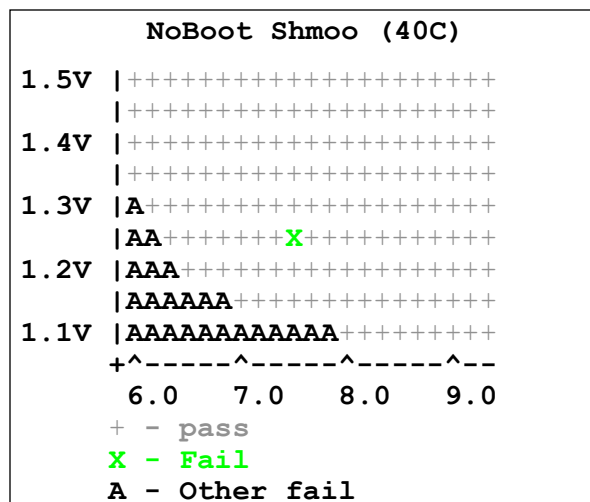





## Vcc Shmoo (10000x repeat)

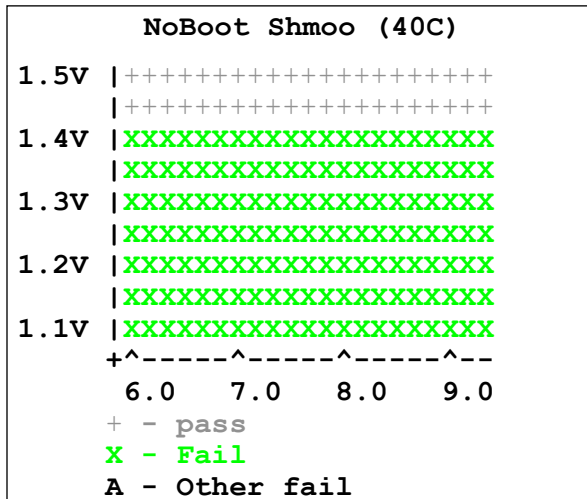

## Temperature Shmoo (10000x repeat)

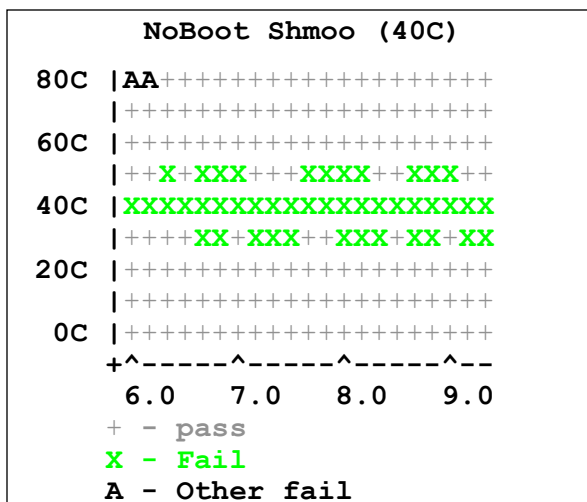


## Scan Analysis

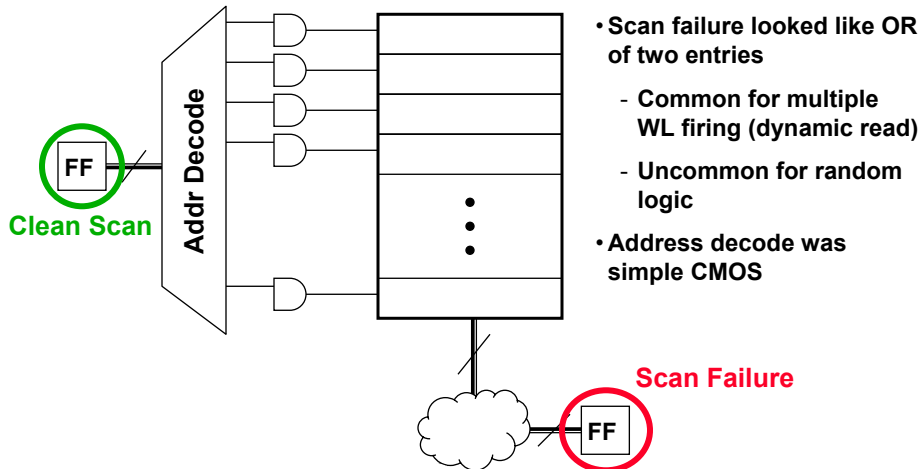

## Wordline Driver


- Used a fancy self-resetting mechanism
  - Self-reset WL prevented read→write min-delay
  - Pulsed WL read array for short period of time

Feedback inverter

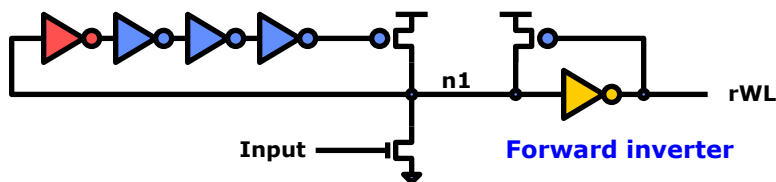
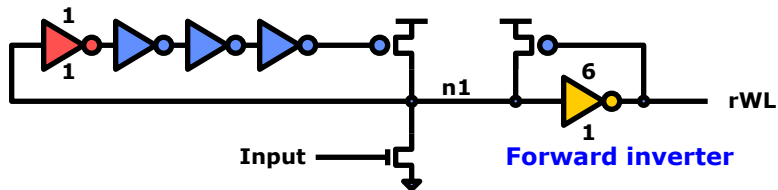
## Wordline Driver: Problem

- Self-reset sized diff't than forward path
  - Initial state could flip forward inverter but not feedback (pseudo-metastable state)
- Resolving pseudo-meta state
  - Access WL
  - High temp
  - Low temp



## Summary

## Summary

---

- Debug requires a lot of detective work
  - Review all the evidence
  - Develop experiments to eliminate possible problems
  - Develop theory of failure
  - Validate theory
- Can't ignore ANY evidence
  - If something doesn't fit, you're missing something
- EVERY problem is different
  - Need to constantly think about alternative methods of validation
    - The Norwegian capacitor
    - The Kleveland voltmeter