

VLSI Systems Designs(SoC DM): Final Exam (2016 Fall)

10:30 ~ 11:50, 12/14/2014, Prof. Jinsang Kim

Assume that a matched unit inverter has widths of 45nm for nMOS and 90nm for pMOS, respectively. The 45nm process technology uses the following parameters unless stated otherwise: $V_{DD} = 1V$, $V_{to} = 0.3V$, $\beta_n = 1mA/V^2$, $\Phi_s = 0.6V$, $\gamma = 0.3V^{0.5}$, $\lambda = 0.02$, $\tau = 3RC = 3ps$

1. (35pts) You need to decide the minimum delay and widths of logic gates in the following circuit. Input and output capacitances are denoted based on a unit matched inverter (5u gate width means width is 5 times larger than that of the unit matched inverter). ND3 = 3 input NAND, NR2 = 2 input NOR, I = Inverter, respectively.




- calculate the logical efforts of all logic gates (ND3, NR2, and I) on the path "A" ~ "Z". (6pts)
- calculate path logical effort, path electrical effort and total path effort of the path "A" ~ "Z"(6pts)
- what are the stage efforts of ND3, NR2 and I for the minimum delay of the path "A" ~ "Z" (3pts)
- determine the widths of ND3, NR2 and I (6pts)
- assume that you need to change the above 3-stage logic into one-stage compound logic. Design the compound logic and compare the delay of the compound logic with the above 3-stage logic (14pts)

Use the following parameters for the following questions.

	setup time	clk-to-Q delay	D-to-Q delay	contamination delay	hold time	clock skew
FF	65 ps	50 ps	n/a	35 ps	30 ps	50 ps
latches	25 ps	50 ps	40 ps	35 ps	30 ps	50 ps

- (15pts) For each of the following sequencing styles, determine the maximum logic propagation delay in each cycle (or half-cycle, for two-phase latches).
 - FFs
 - two-phase transparent latches with 60ps of nonoverlap between phases
- (17 pts) You need to add testability for a two-bit adder sequencing block using FFs. Draw the RTL level architecture including testability of all the sequential and combinational blocks.
- (5pts) Try to generate a test vector based on the SA1 fault model at ϕ .

 

- (28pts) Draw the architecture of a PLL which multiplies frequency by N times at S domain. Also, derive the transfer equations of each sub-block and the corresponding circuit.

- END -