

Circuit Pitfalls


Circuit Pitfalls

- ❑ Detective puzzle
 - Given circuit and symptom, diagnose cause and recommend solution
 - All these pitfalls have caused failures in real chips

Bad Circuit 1

❑ Circuit

- 2:1 multiplexer

 

❑ Principle:

-
-
-

❑ Solution:


❑ Symptom

- Mux works when selected D is 0 but not 1.
- Or fails at low V_{DD} .
- Or fails in SFSF corner.

Bad Circuit 2

❑ Circuit

- Latch

 

❑ Symptom

- Load a 0 into Q
- Set $\phi = 0$
- Eventually Q spontaneously flips to 1

❑ Principle:


-
-

❑ Solution:

Bad Circuit 3

❑ Circuit

- Domino AND gate

 

❑ Symptom

- Precharge gate ($Y=0$)
- Then evaluate
- Eventually Y spontaneously flips to 1

❑ Principle:


-
-

❑ Solution:

Bad Circuit 4

❑ Circuit

- Pseudo-nMOS OR

 

❑ Symptom

- When only one input is true, $Y = 0$.
- Perhaps only happens in SF corner.

❑ Principle:


–
–

❑ Solution:

Bad Circuit 5

❑ Circuit

- Latch

 

❑ Principle:

–

❑ Solutions:


❑ Symptom

- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.

Bad Circuit 6

❑ Circuit

- Domino AND gate

 

❑ Principle:

–

❑ Solutions:


❑ Symptom

- Precharge gate while $A = B = 0$, so $Z = 0$
- Set $\phi = 1$
- A rises
- Z is observed to sometimes rise

Bad Circuit 7

❑ Circuit

- Dynamic gate + latch

 

❑ Principle:

–

❑ Solution:


❑ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

Bad Circuit 8

❑ Circuit

- Latch

 

❑ Symptom

- Q changes while latch is opaque
- Especially if D comes from a far-away driver

❑ Principle:

-
-


❑ Solution:

Summary

- ❑ Causes of circuit pitfalls
 - Threshold drops, ratio failures, leakage, charge sharing, power supply noise, coupling, diffusion input noise sensitivity, race conditions, hot spots, soft errors, process (corner) sensitivity,
 - Metastability
 - Minority carrier injection
 - Back-gate coupling
 - Delay matching


Back-gate Coupling

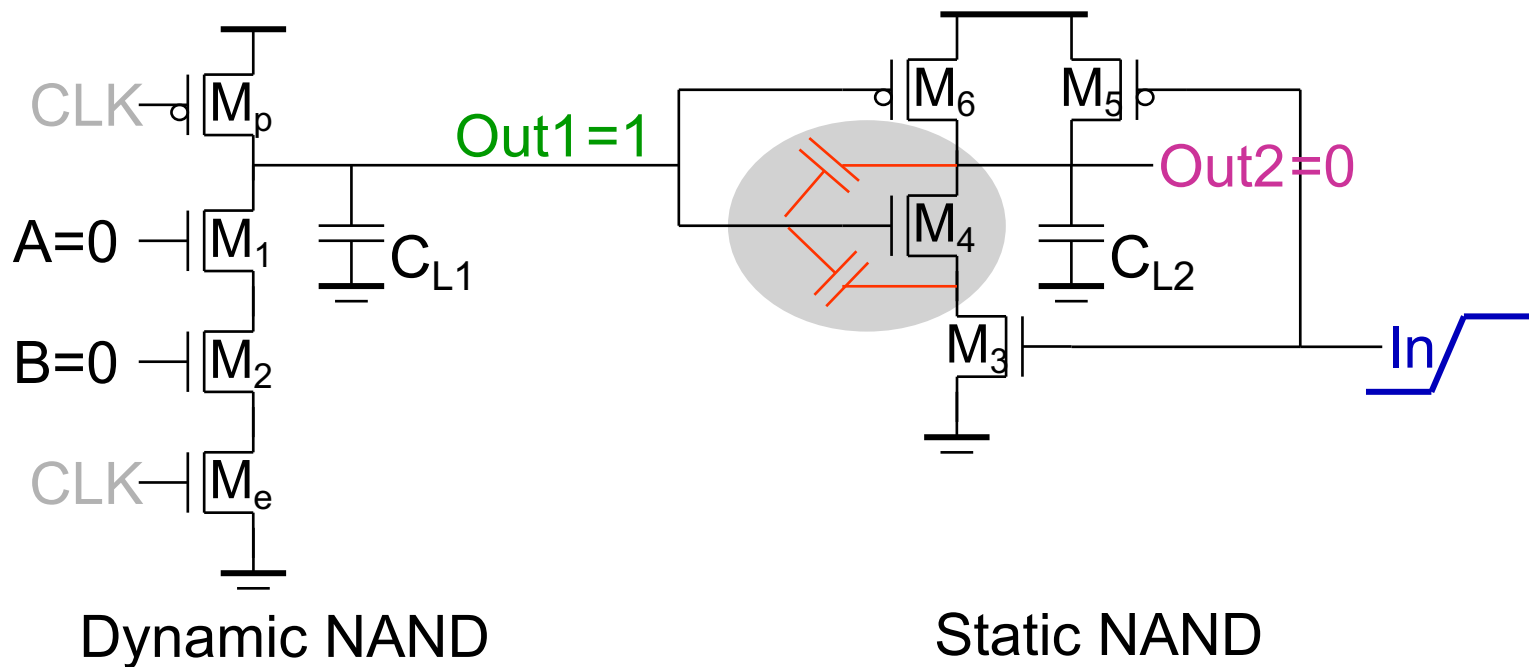- Susceptible to crosstalk due to 1) high impedance of the output node and 2) backgate capacitive coupling
 - **Out2** capacitively couples with **Out1** through the gate-source and gate-drain capacitances of M4




Back-gate Coupling

 - Capacitive coupling means **Out1** drops significantly so **Out2** doesn't go all the way to ground





Clock Feedthrough

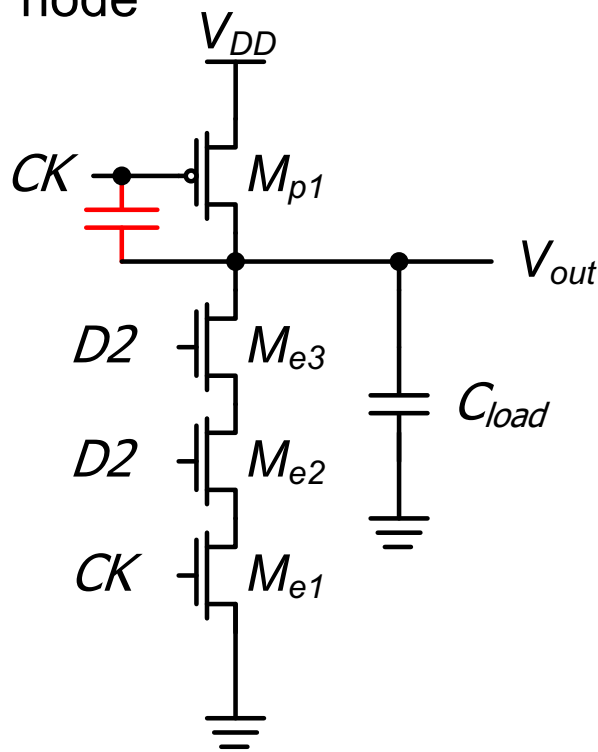- A special case of backgate capacitive coupling between the clock input of the precharge transistor and the dynamic output node



- Coupling between output node and CK input of the precharge device due to the gate-drain capacitance. So V_{out} can rise above V_{DD} . The fast rising (and falling edges) of the clock **couple** to output.

Clock Feedthrough

  

Summary

- ❑ Static CMOS gates are very robust
 - Will settle to correct value if you wait long enough
- ❑ Other circuits suffer from a variety of pitfalls
 - Tradeoff between performance & robustness
- ❑ Essential to check circuits for pitfalls
 - For large chips, you need an automatic checker.
 - Design rules aren't worth the paper they are printed on unless you back them up with a tool.