

# **Chap. 12: Clocking, PLLs and DLLs**


# Outline

---

- ☐ Clock Recovery
- ☐ Clock System Architecture
- ☐ Phase-Locked Loops
- ☐ Delay-Locked Loops
- ☐ Clock Distribution
- ☐ High Speed Links
- ☐ Synchronizer

 
# Source-Synchronous Clocking

- ❑ Send clock with the data
- ❑ Flight times roughly match each other
  - Transmit on falling edge of tclk
  - Receive on rising edge of rclk



 
# Single vs. Double Data Rate

- ❑ In ordinary single data rate (SDR) system, clock switches twice as often as the data




 - ❑ If the system can handle this speed clock, the data is running at half the available bandwidth
- ❑ In double-data-rate (DDR) transmit and receive on both edges of the clock


 
# Phase Alignment

- ❑ If the DDR clock is aligned to the transmitted clock, it must be shifted by  $90^\circ$  before sampling
- ❑ Use PLL





# Mesochronous Clocking

- ❑ As speeds increase, it is difficult to keep clock and data aligned
  - Mismatches in trace lengths
  - Mismatches in propagation speeds
  - Different in clock vs. data drivers
- ❑ Mesochronous: clock and data have same frequency but unknown phase
  - Use PLL/DLL to realign clock to each data channel
 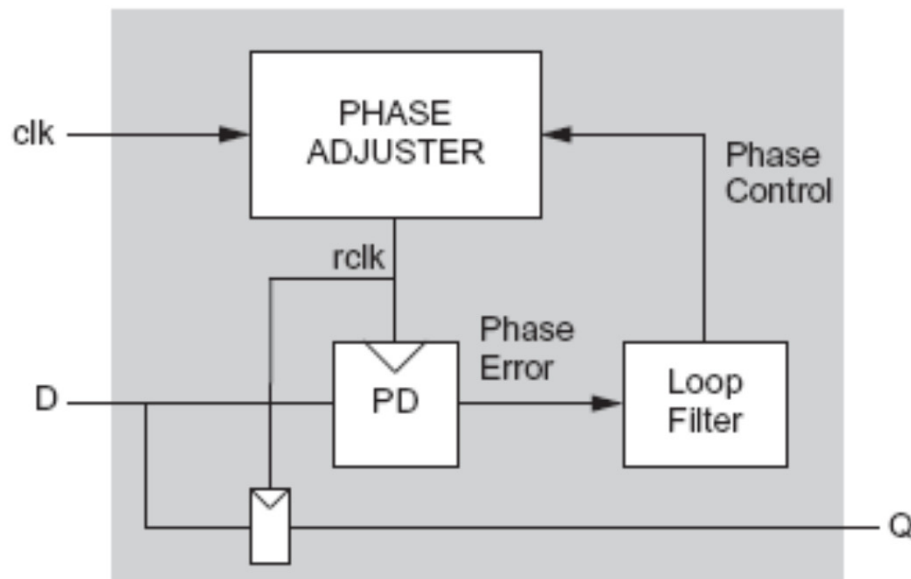
# Phase Calibration Loop

- ❑ Special phase detector compares clock & data phase



# Clock Generation


- ❑ Low frequency:
  - Buffer input clock and drive to all registers
- ❑ High frequency
  - Buffer delay introduces large skew relative to input clocks
    - Makes it difficult to sample input data
  - Distributing a very fast clock on a PCB is hard




# Zero-Delay Buffer

- ❑ If the periodic clock is delayed by  $T_c$ , it is indistinguishable from the original clock
- ❑ Build feedback system to guarantee this delay

## Phase-Locked Loop (PLL)

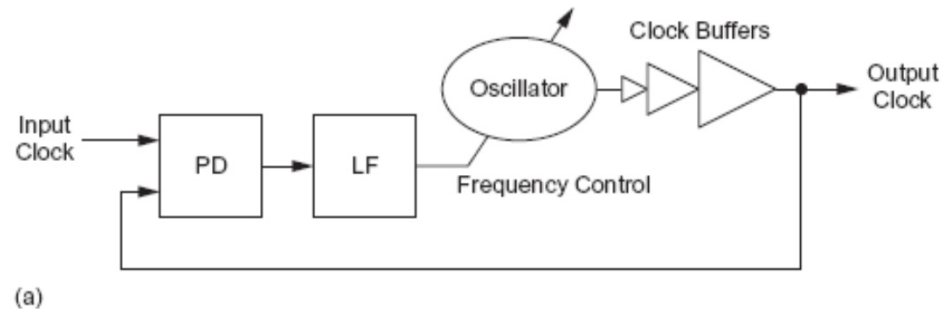


## Delay-Locked Loop (PLL)

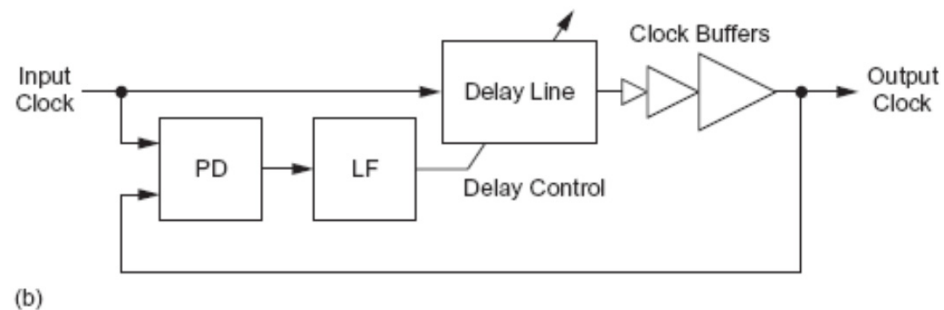
 
# Frequency Multiplication

- ❑ PLLs can multiply the clock frequency




# Phase and Frequency

- Analyze PLLs and DLLs in term of phase  $\Phi(t)$  rather than voltage  $v(t)$

$$\text{clk} = \begin{cases} 1 & \Phi(t) \bmod 2\pi < \pi \\ 0 & \Phi(t) \bmod 2\pi \geq \pi \end{cases}$$

$$\Phi(t) = 2\pi \int_0^t f(t) dt$$

 

- Input and output clocks may deviate from locked phase
  - Small signal analysis

$$\Phi_{\text{in}}(t) = \Phi(t) + \Delta\Phi_{\text{in}}(t)$$


$$\Phi_{\text{out}}(t) = N\Phi(t) + \Delta\Phi_{\text{out}}(t)$$

# Linear System Model


- ❑ Treat PLL/DLL as a linear system
  - Compute deviation of desired freq. from locked position
  - Assume small deviations from locked
  - Treat system as linear for these small changes
- ❑ Analysis is not valid far from lock
  - e.g. during acquisition at startup
- ❑ Continuous time assumption
  - PLL/DLL is really a discrete time system
    - Updates once per cycle
  - If the bandwidth  $\ll 1/10$  clock freq, treat as continuous
- ❑ Use Laplace transforms and standard analysis of linear continuous-time feedback control systems

# Phase-Locked Loop (PLL)

## □ System

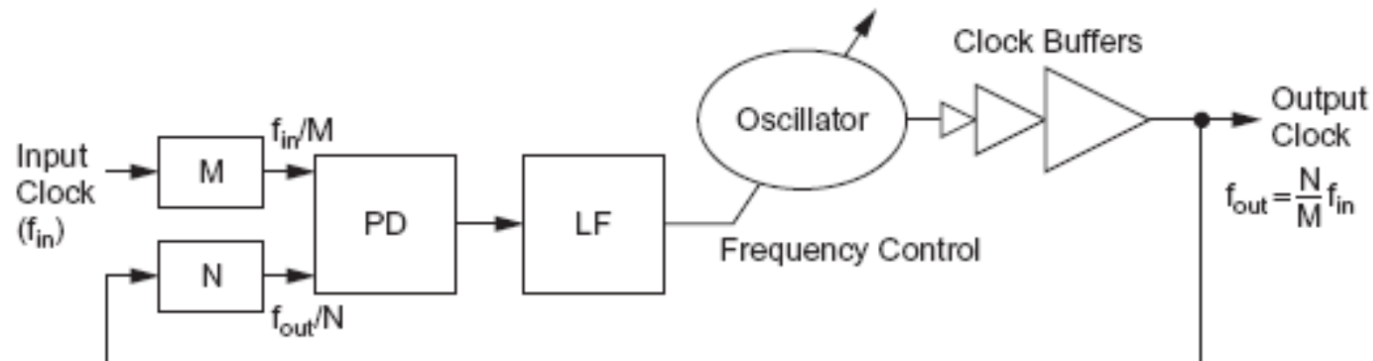


## □ Linear Model

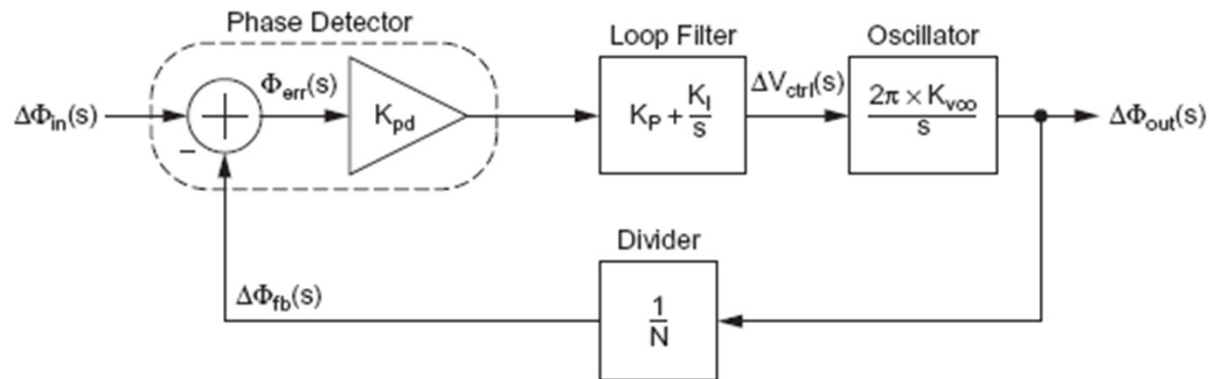

# Voltage-Controlled Oscillator


□ VCO

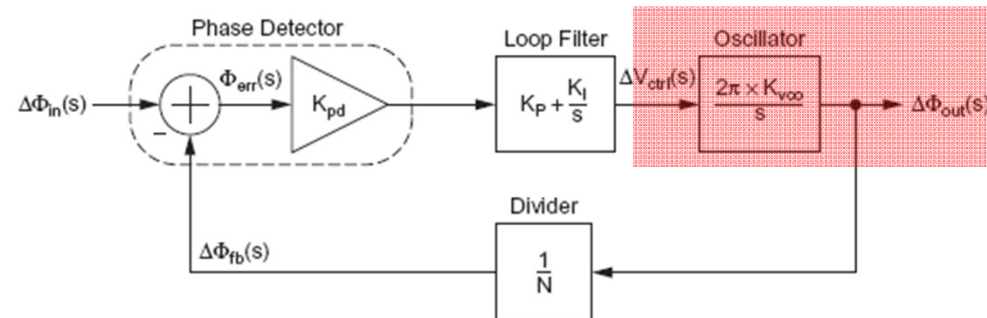


$$V_{ctrl}(t) = V_{ctrl0} + \Delta V_{ctrl}(t)$$

$$\frac{\Delta f_{out}}{\Delta V_{ctrl}} = K_{vco}$$
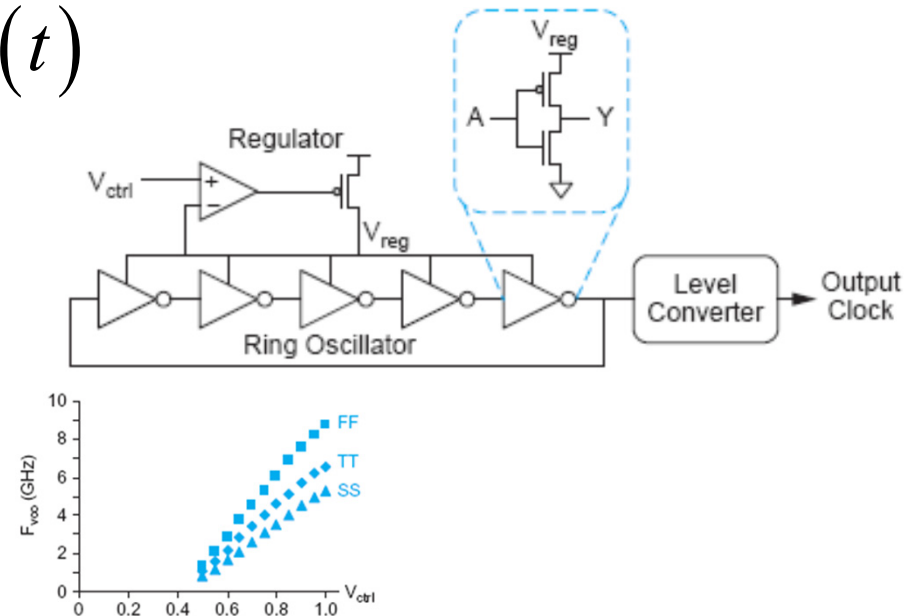
$$\frac{\Delta\Phi_{out}(s)}{\Delta V_{ctrl}(s)} = \frac{2\pi K_{vco}}{s}$$




# Alternative Delay Elements

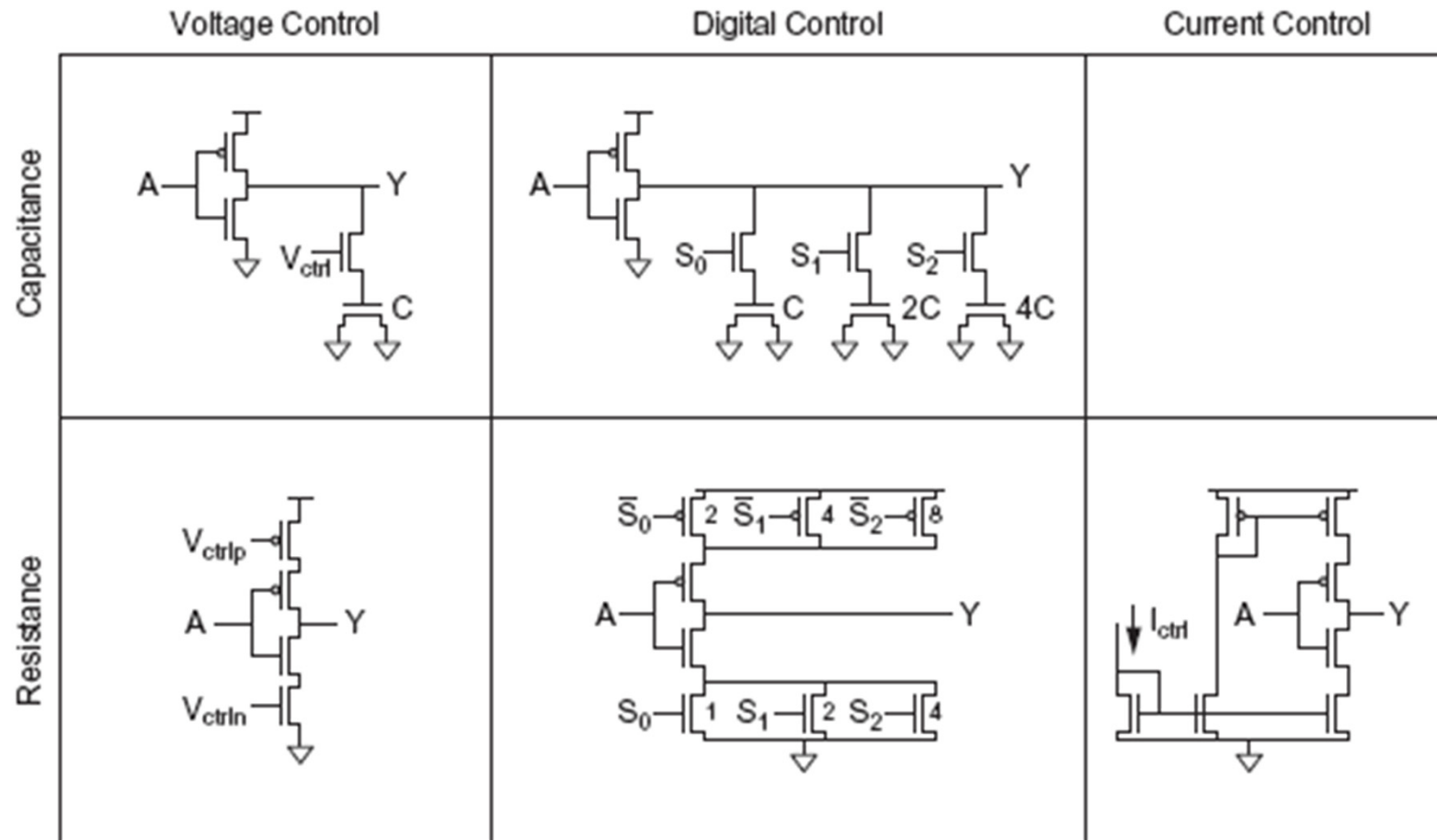
 
# Frequency Divider

- Divide clock by N
  - Use mod-N counter




$$\Delta f_{fb} = \frac{\Delta f_{out}}{N}$$

$$\Delta\Phi_{fb} = \frac{\Delta\Phi_{out}}{N}$$




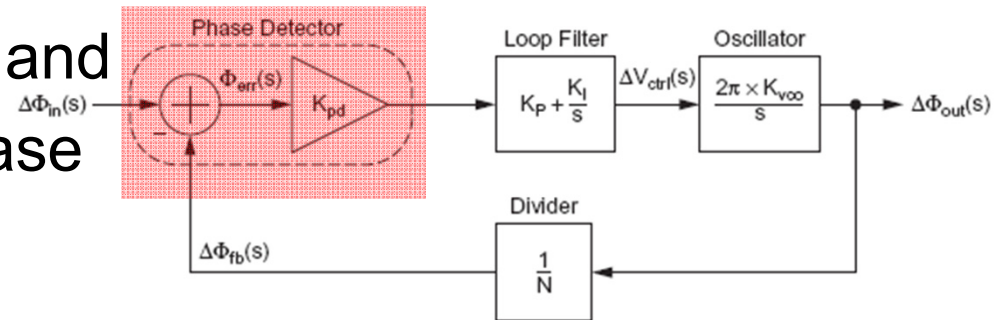
# Phase Detector

- ❑ Difference of input and feedback clock phase



  
- ❑ Often built from phase-frequency detector (PFD)


 
# Phase Detector


- ❑ Convert up and down pulses into current proportional to phase error using a charge pump

$$\frac{I_{pd}(s)}{\Phi_{err}(s)} = \frac{I_{cp}}{2\pi} = K_{pd}$$



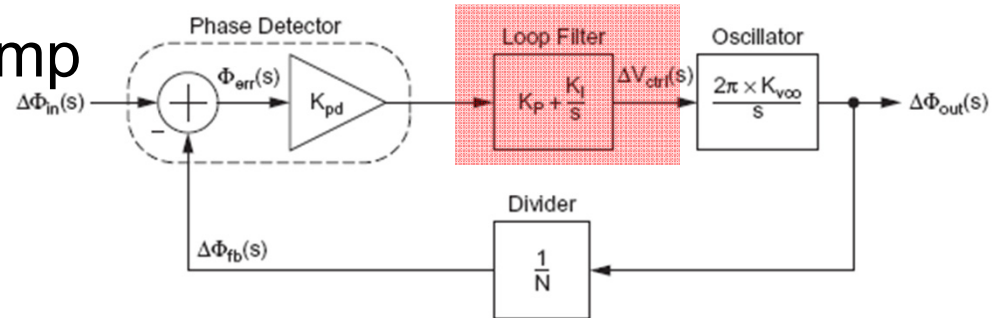
# Loop Filter

- ❑ Convert charge pump current into  $V_{ctrl}$



- ❑ Use proportional-integral control (PI) to generate a control signal dependent on the error and its integral
  - Drives error to 0
 
$$\frac{V_{ctrl}(s)}{I_{pd}(s)} = \frac{1}{sC} + R$$



# PLL Loop Dynamics

- ❑ Closed loop transfer function of PLL

$$H(s) = \frac{\Delta\Phi_{\text{out}}(s)}{\Delta\Phi_{\text{in}}(s)} = \frac{K_{pd} \left( R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}{1 + \frac{1}{N} K_{pd} \left( R + \frac{1}{sC} \right) \frac{2\pi K_{\text{vco}}}{s}}$$

- ❑ This is a second order system

$$H(s) = N \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \omega_n = \sqrt{\frac{I_{cp} K_{\text{vco}}}{NC}} \quad \zeta = \frac{\omega_n}{2} RC$$


- ❑  $\omega_n$  indicates loop bandwidth
- ❑  $\zeta$  indicates damping; choose 0.7 – 1 to avoid ringing

# Delay Locked Loop


- ❑ Delays input clock rather than creating a new clock with an oscillator
- ❑ Cannot perform frequency multiplication
- ❑ More stable and easier to design
  - 1<sup>st</sup> order rather than 2<sup>nd</sup>
- ❑ State variable is now time (T)
  - Locks when loop delay is exactly  $T_c$
  - Deviations of  $\Delta T$  from locked value

# Delay-Locked Loop (DLL)

## □ System

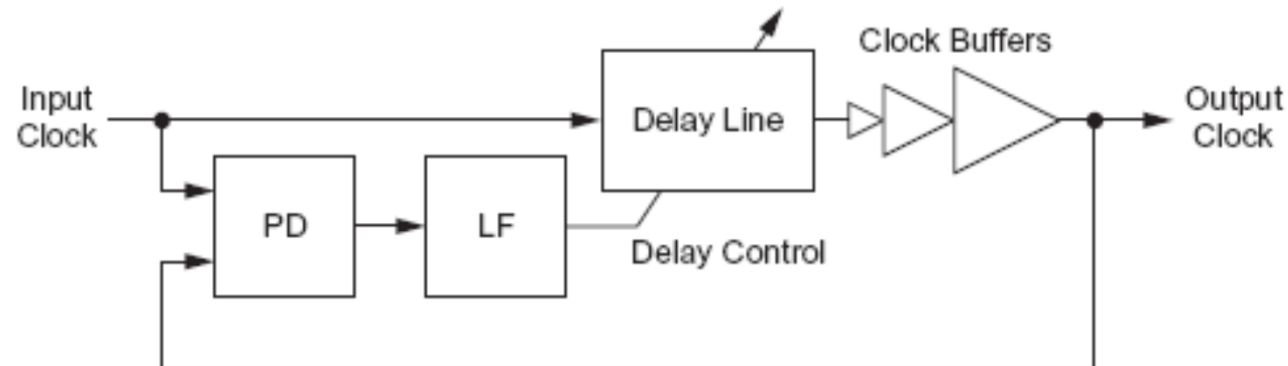


## □ Linear Model

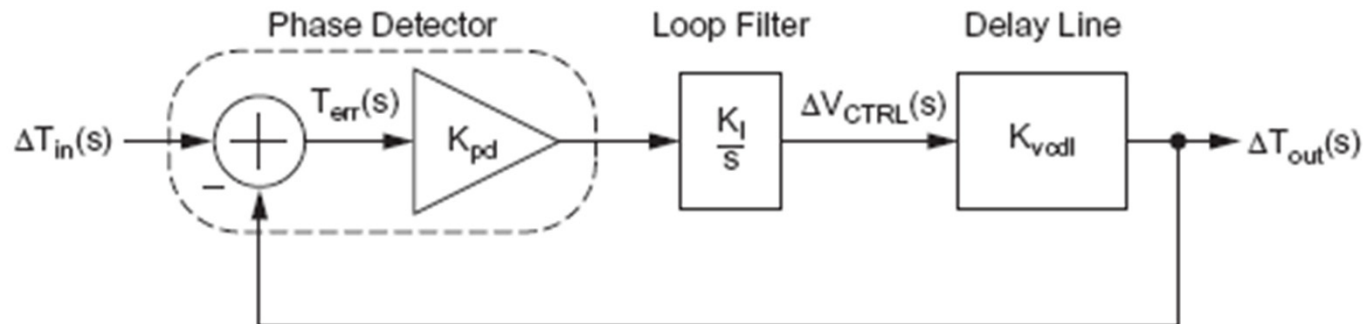


# Delay Line

- Delay input clock

 


- Typically use voltage-controlled delay line
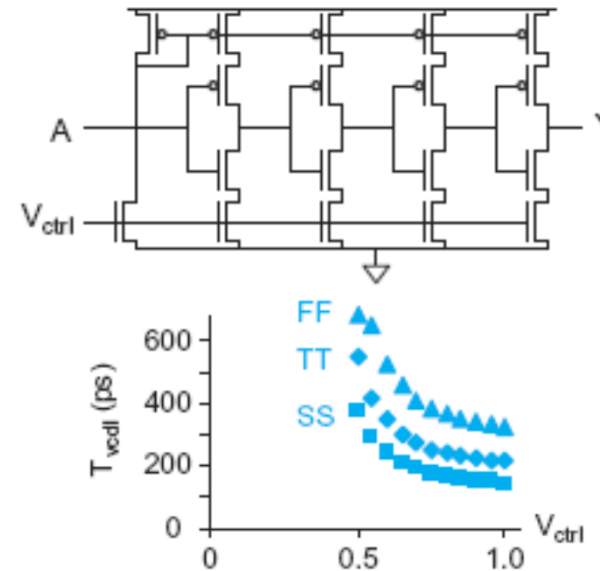
$$\frac{\Delta T_{out}(s)}{\Delta V_{ctrl}(s)} = K_{vcdl}$$



# Phase Detector

- ❑ Detect phase error

 


- ❑ Typically use PFD and charge pump, as in PLL

$$\frac{I_{pd}(s)}{T_{err}(s)} = \frac{I_{cp}}{T_c}$$



 
# Loop Filter

- ❑ Convert error current into control voltage



- ❑ Integral control is sufficient
- ❑ Typically use a capacitor as the loop filter
 
$$\frac{\Delta V_{\text{ctrl}}(s)}{I_{pd}(s)} = \frac{K_I}{s} = \frac{1}{sC}$$



# DLL Loop Dynamics

- ❑ Closed loop transfer function of DLL

$$H(s) = \frac{\Delta T_{\text{out}}(s)}{\Delta T_{\text{in}}(s)} = \frac{1}{s\tau + 1}$$

- ❑ This is a first order system

$$\tau = \frac{1}{K_{pd}K_IK_{vc dl}} = \frac{CT_c}{I_{cp}K_{vc dl}}$$


- ❑  $\tau$  indicates time constant (inverse of bandwidth)
  - Choose at least  $10T_c$  for continuous time approx.

# Clock Distribution

- ❑ On a small chip, the clock distribution network is just a wire
  - And possibly an inverter for  $\text{clk}_b$
- ❑ On practical chips, the RC delay of the wire resistance and gate load is very long
  - Variations in this delay cause clock to get to different elements at different times
  - This is called *clock skew*
- ❑ Most chips use repeaters to buffer the clock and equalize the delay
  - Reduces but doesn't eliminate skew
 
# Example

- ❑ Skew comes from differences in gate and wire delay
  - With right buffer sizing,  $\text{clk}_1$  and  $\text{clk}_2$  could ideally arrive at the same time.
  - But power supply noise changes buffer delays
  - $\text{clk}_2$  and  $\text{clk}_3$  will always see RC skew




# Review: Skew Impact

- ❑ Ideally full cycle is available for work
- ❑ Skew adds sequencing overhead
- ❑ Increases hold time too

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
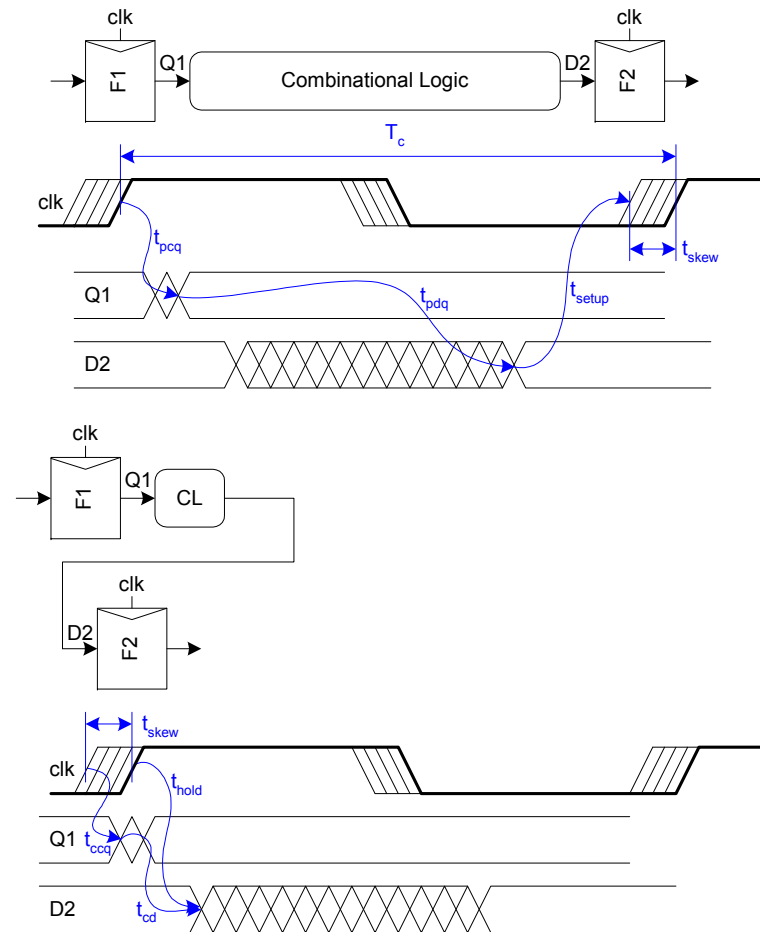
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



# Solutions

- ❑ Reduce clock skew
  - Careful clock distribution network design
  - Plenty of metal wiring resources
- ❑ Analyze clock skew
  - Only budget actual, not worst case skews
  - Local vs. global skew budgets
- ❑ Tolerate clock skew
  - Choose circuit structures insensitive to skew

# Clock Dist. Networks

---

- ☐ *Ad hoc*
- ☐ Grids
- ☐ H-tree
- ☐ Hybrid


# Clock Grids

- ☐ Use grid on two or more levels to carry clock
- ☐ Make wires wide to reduce RC delay
- ☐ Ensures low skew between nearby points
- ☐ But possibly large skew across die




# Alpha Clock Grids





Alpha 21064

 


Alpha 21164

 


Alpha 21264

    

Alpha 21064

 


Alpha 21164

 

Alpha 21264

 
# H-Trees

- ❑ Fractal structure
  - Gets clock arbitrarily close to any point
  - Matched delay along all paths
- ❑ Delay variations cause skew
- ❑ A and B might see big skew


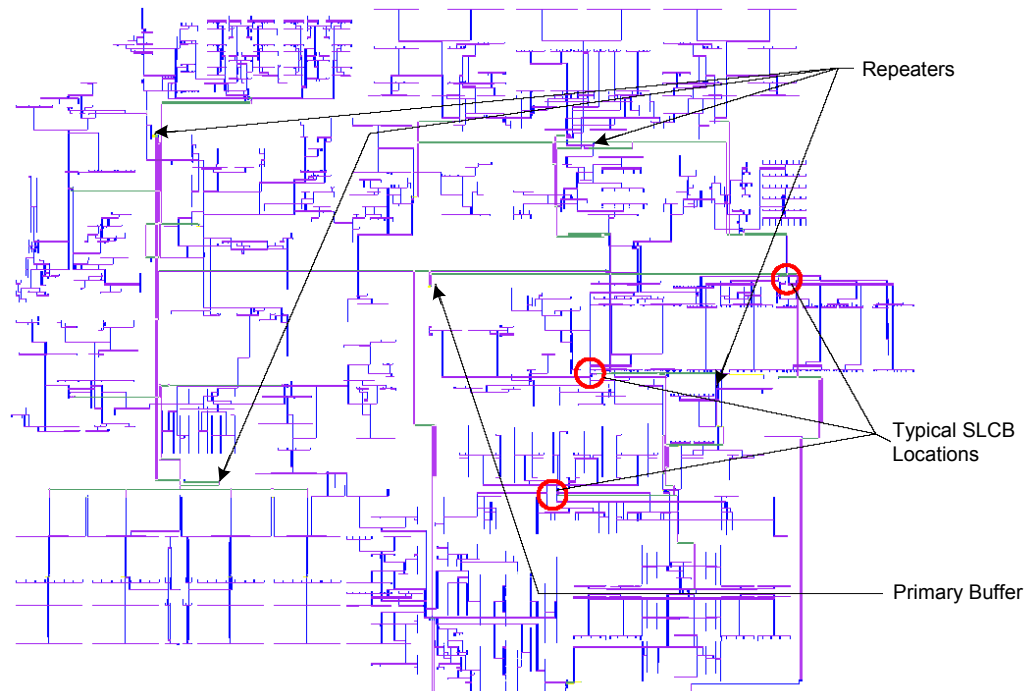
# Itanium 2 H-Tree

- ❑ Four levels of buffering:
  - Primary driver
  - Repeater
  - Second-level clock buffer
  - Gater
- ❑ Route around obstructions



# Hybrid Networks

- ❑ Use H-tree to distribute clock to many points
- ❑ Tie these points together with a grid
  
- ❑ Ex: IBM Power4, PowerPC
  - H-tree drives 16-64 sector buffers
  - Buffers drive total of 1024 points
  - All points shorted together with grid





# High-Speed I/O

- ☐ Transmit data faster than the flight time along the line
- ☐ Transmitters must generate very short pulses
- ☐ Receivers must be accurately synchronized to detect the pulses

# High Speed Transmitters

- ❑ How to handle termination?
  - High impedance current-mode driver + load term?
  - Or low-impedance driver + source termination
- ❑ Single-ended vs. differential
  - Single-ended uses half the wires
  - Differential is Immune to common mode noise
- ❑ Pull-only vs. Push-Pull
  - Pull-only has half the transistors
  - Push-pull uses less power for the same swing

# High-Speed Transmitters

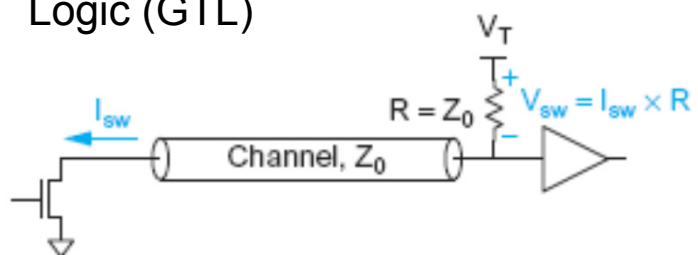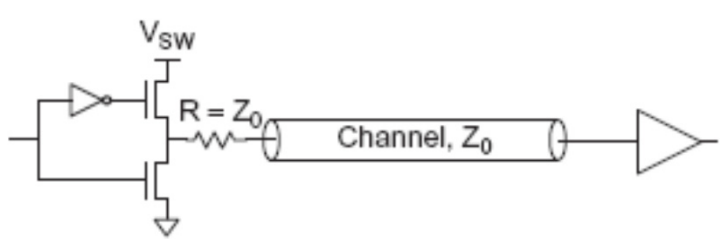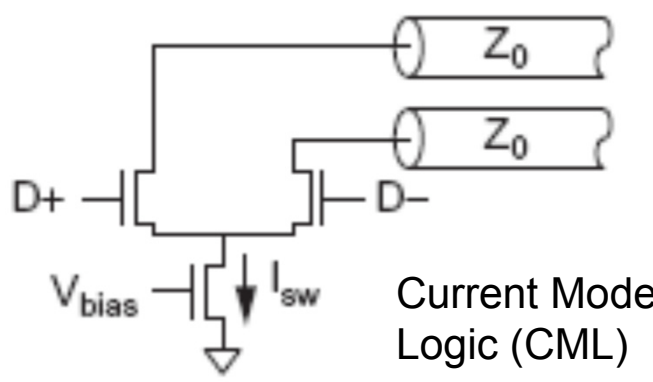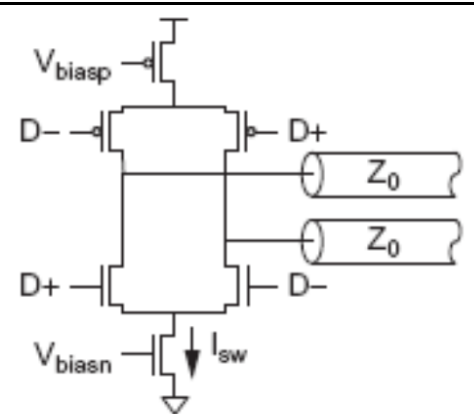	Pull-Only	Push-Pull
Single-Ended	<p>Gunning Transceiver Logic (GTL)</p>  <p><math>R = Z_0</math>, <math>V_T</math>, <math>V_{sw} = I_{sw} \times R</math></p>	 <p><math>V_{sw}</math>, <math>R = Z_0</math>, Channel, <math>Z_0</math></p>
Differential	 <p>Current Mode Logic (CML)</p> <p><math>V_{bias}</math>, <math>I_{sw}</math>, <math>Z_0</math></p>	 <p>Low-Voltage Differential Signalling (LVDS)</p> <p><math>V_{biasp}</math>, <math>V_{biasn}</math>, <math>I_{sw}</math>, <math>Z_0</math></p>

# High-Speed Receivers

- ❑ Sample data in the middle of the bit interval
- ❑ How do we know when?

