 


# VLSI Systems Designs: Midterm Exam (2015 Fall)

11/14/2014, Prof. Jinsang Kim

*Assume that a matched unit inverter has widths of 45nm for nMOS and 90nm for pMOS, respectively. The 45nm process technology uses the followings unless stated otherwise:  $V_{DD} = 1V$ ,  $V_{to} = 0.3V$ ,  $\beta_n = 1mA/V^2$ ,  $\Phi_s = 0.6V$ ,  $\gamma = 0.3V^{0.5}$ ,  $\lambda = 0.02$ ,  $\tau = 3RC = 3ps$ , electron velocity =  $10^5 cm/s$*

1. (10 pts) A metal2 wire is 1um long and  $2\lambda$  wide with  $R = 0.08 \Omega/\square$ ,  $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m}$ . A two-input NAND gate drives a 3X receiver inverter through the above wire. Estimate the delay between two gates when the output of the NAND gate changes from '1' to '0'. Gate capacitance of a unit inverter is  $C = 2\text{fF}/\mu\text{m}$  and resistances of both nMOS and pMOS are  $R = 2.5 K\Omega \cdot \mu\text{m}$ .
2. (7pts) Design a low-skewed two input CMOS AND gate. Also, verify why the gate is low-skewed.
3. (13pts) Design a high skewed two input domino OR gate and decide the logical effort and the parasitic delay.
4. (10pts) Analyze the symptom and its principle. Also, suggest a solution.



5. (10pts) Show that how much time we can borrow by drawing the timing corresponding diagram when we use 2-phase latches.
6. (50pts) Let's design a simple half adder sequencing block using buffered flip-flops. And then, analyze the timing information. Assume that there is no clock skew and T-gate input capacitance is 10C. Let's take a step-by-step approach as followings.
  - a) (8pts) design the buffered FF at the transistor level.
  - b) (14pts) estimate the clock-to-Q delay, setup time and hold time of the FF. T-gate delay can be simply modeled as the traveling time of main carriers between source and drain of the nMOS transistor.
  - c) (14pts) design the half adder ( $S = a \text{ XOR } b$ ,  $C = a \text{ AND } b$ ) at the transistor level and estimate the propagation delay and the contamination delay. Inverted inputs are not available.
  - d) (7pts) determine the maximum operating frequency of this block.
  - e) (7pts) show that this block satisfies the hold time constraint or not.

- END -